

StudentZone— ADALM2000 Activity: Op Amp as Comparator

Doug Mercer, Consulting Fellow
and Antoniu Miclaus, System Applications Engineer

Objective:

In this lab, we introduce the operational amplifier (op amp) in switch-mode configuration needed to obtain an op amp voltage comparator's behavior. The voltage comparator circuit's purpose is to highlight the relative state of the two-input voltage via two different states of the output voltage. The comparison is made using the sign of the difference between the two input voltages, while response is one of the two possible output values, dependent on the sign of that specific difference.

For an op amp comparator, we can consider a single input V_0 as the difference between V_+ and V_- . Therefore, the output voltage V_0 can get one of the two possible values:

- ▶ $V_0 = V_{OH}$ (high), meaning that $V_+ > V_-$ ($v_0 > 0$)
- ▶ $V_0 = V_{OL}$ (low), meaning that $V_+ < V_-$ ($v_0 < 0$)

We consider the threshold voltage V_{Th} as the particular value (or values) of the input voltage v_i for which the switching at the output takes place (setting $V_0 = 0$).

Two main types of voltage comparators are to be considered:

- ▶ Simple comparators: without feedback and with only one threshold voltage.
- ▶ Hysteresis comparators: with positive feedback and two threshold voltages.

Materials:

- ▶ ADALM2000 active learning module
- ▶ Solderless breadboard and jumper wire kit
- ▶ Three 10 kΩ resistor
- ▶ One 20 kΩ resistor
- ▶ One OP97 (low slew rate amplifier supplied with recent versions of the ADALP2000 analog parts kit) or OP37

Simple Comparator

Background:

The high intrinsic gain of the op amp and the output saturation effects can be exploited by configuring the op amp as a comparator as in Figure 1. This is essentially a binary-state decision-making circuit: if the voltage at the positive (+) terminal is greater than the voltage at the negative (−) terminal, $V_{IN} > V_{REF}$, the output goes high (saturates at its maximum value). Conversely, if $V_{IN} < V_{REF}$, the output goes low. The circuit compares the voltages at the two inputs and generates an output based on the relative values. Unlike all the previous circuits, there is no feedback between the input and output; we say that the circuit is operating open-loop.

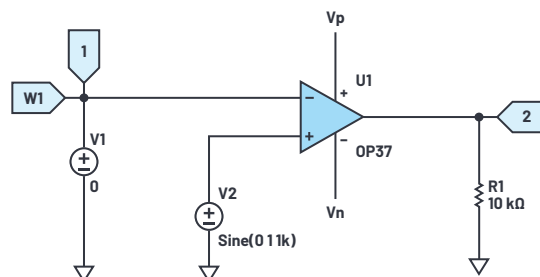


Figure 1. Op amp as comparator.

Hardware Setup:

Comparators are used in different ways, and we will see them in action in future labs. Here we will use the comparator in a common configuration that generates a square wave with a variable pulse width.

Start by shutting off the power supplies and assemble the circuit. As with the summing amplifier circuit, use the second waveform generator output for the dc source V_{REF} and turn the amplitude to zero and the output offset all the way down so that you can adjust up from zero during the experiment.

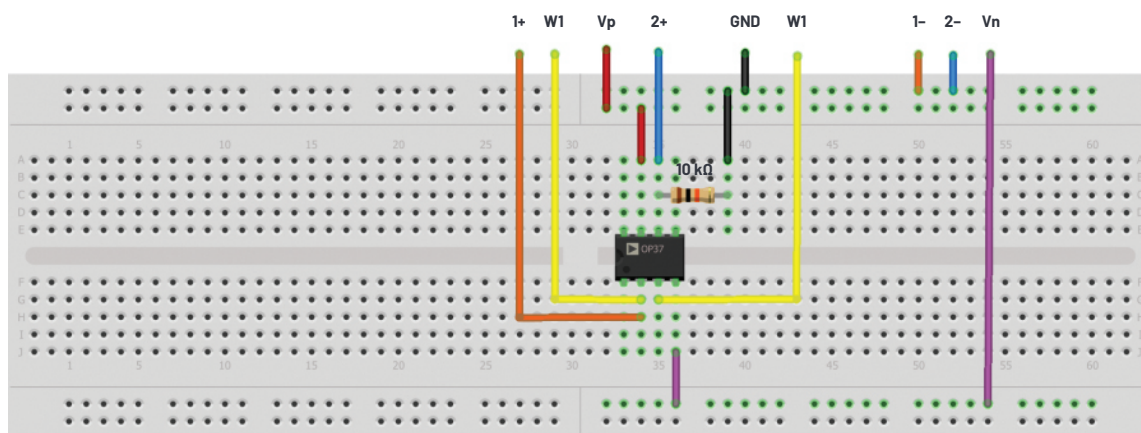


Figure 2. Comparator breadboard circuit.

Configure the waveform generator V_{IN} for a 2 V amplitude peak-to-peak sine wave at 1 kHz. With the power supply on and V_{REF} at zero volts, export the output waveform.

Now slowly increase V_{REF} and observe what happens. Record the output waveform for $V_{REF} = 1$ V. Keep increasing V_{REF} until it exceeds 2 V and observe what happens. Can you explain this?

Repeat the previous step for a triangular input waveform and record your observations for your lab report.

Procedure:

Use the first waveform generator as source V_{IN} to provide a 2 V amplitude peak-to-peak, 1 kHz sine wave excitation to the circuit. Supply the op amp to ± 5 V from the power supply. Configure the scope so that the input signal is displayed on Channel 1 and the output signal is displayed on Channel 2.

A plot example is presented in Figure 3.



Figure 3. Comparator waveforms.

Hysteresis Comparator

Hysteresis is the dependence of a system's current state on previous values of quantities determining said current state. The output value is not a strict function of the corresponding input, but also incorporates some lag, delay, or history dependence. In particular, the response for a decrease in the input variable is different from the response for an increase in the input variable.

In this configuration, there are two threshold values V_{THH} and V_{THL} with two output values V_{OH} and V_{OL} . The threshold values should depend on the output value, which is fed back to the input and contributes to the threshold values (positive feedback). Via a resistive divider, a fraction of the output voltage is fed back to the noninverting input.

When analyzing hysteresis comparators, we must take into consideration the moving direction of the hysteresis and the fact that, at a certain moment, only one threshold is active.

The input signal triggers the switching of the output, with the switching process being sustained by the positive feedback.

Noninverting Hysteresis Comparator

Background:

Consider the circuit presented in Figure 4.

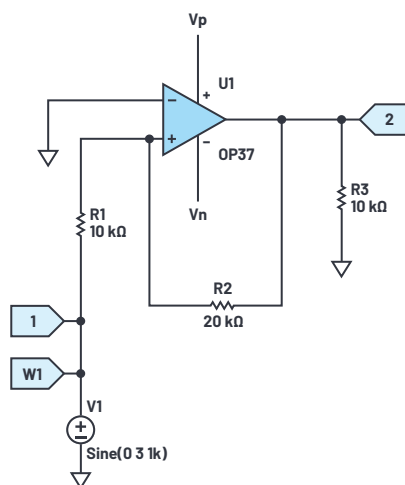


Figure 4. Noninverting hysteresis comparator.

For the noninverting hysteresis comparator circuit in Figure 4, V_{IN} is applied to the noninverting input of the op amp. Resistors R1 and R2 form a voltage divider network across the comparator, providing the positive feedback with part of the output voltage appearing at the noninverting input along with the V_{IN} via the same resistive divider.

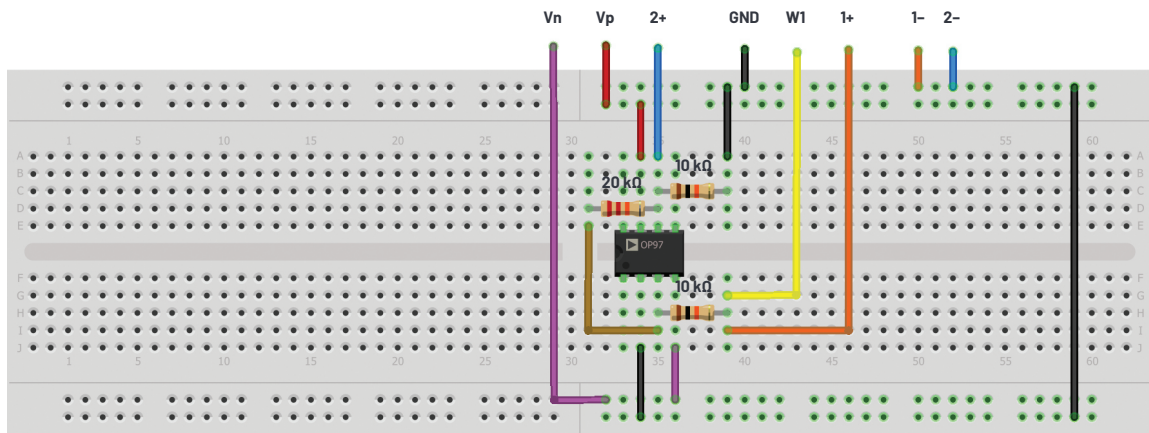


Figure 5. Noninverting hysteresis comparator breadboard circuit.

The amount of feedback is determined by the resistive ratio of the two resistors used (in this situation, the ratio will be one-half).

We can compute the threshold voltages as follows:

$$v_D = v^+ - v^- = \left(\frac{R1}{R1 + R2} \right) v_{OUT} + \left(\frac{R2}{R1 + R2} \right) V_{IN} - 0 \quad (1)$$

Considering $V_D = 0$, $V_{IN} \rightarrow V_{Th}$, we obtain the following thresholds:

$$V_{ThL} = -\left(\frac{R1}{R2} \right) V_{OH} \quad (2)$$

$$V_{ThH} = -\left(\frac{R1}{R2} \right) V_{OL}$$

Hardware Setup:

Build the following breadboard circuit for the noninverting hysteresis comparator.

Procedure:

Use the first waveform generator as source V_{IN} to provide a 6 V amplitude peak-to-peak, 1 kHz sine wave excitation to the circuit. Supply the op amp to ± 5 V from the power supply. Configure the scope so that the input signal is displayed on Channel 1 and the output signal is displayed on Channel 2.

A plot example is presented in Figure 6.

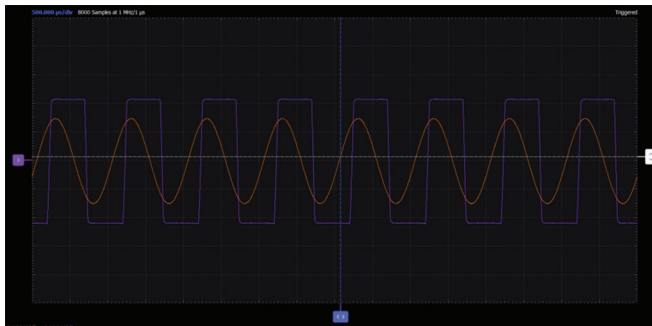


Figure 6. Noninverting hysteresis comparator waveform.

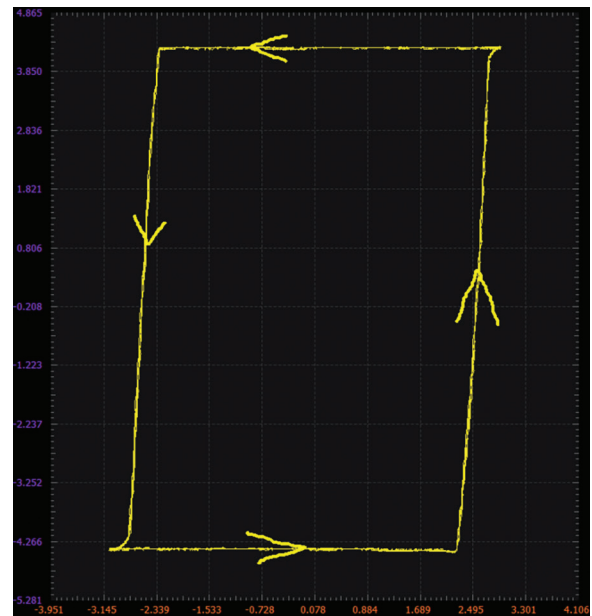


Figure 7. Noninverting hysteresis comparator XY plot.

In Figure 7, you can observe the voltage transfer characteristic of the noninverting hysteresis comparator (the arrows drawn indicate the flow of the signal with respect to the thresholds). Compare the computed threshold voltage values with the measured ones.

Inverting Hysteresis Comparator

Background:

Consider the circuit presented in Figure 8.

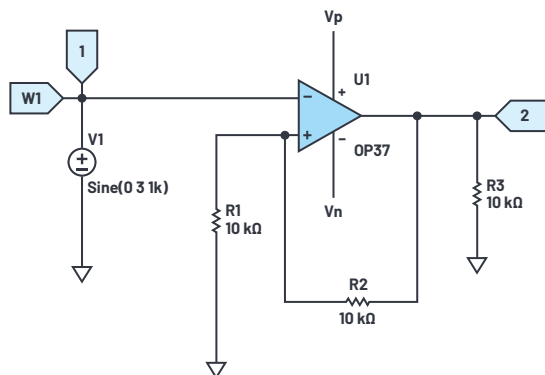


Figure 8. Inverting hysteresis comparator.

For the inverting hysteresis comparator circuit in Figure 8, V_{IN} is applied to the inverting input of the op amp. Resistors R1 and R2 form a voltage divider network across the comparator providing the positive feedback with part of the output voltage appearing at the noninverting input.

The amount of feedback is determined by the resistive ratio of the two resistors used (in this situation, the ratio will be one-half).

We can compute the threshold voltages as follows:

$$v_D = v^+ - v^- = \left(\frac{R1}{(R1 + R2)} \right) v_{OUT} - v_{IN} \quad (3)$$

Considering $V_D = 0$, $V_{IN} \rightarrow V_{Th}$, we obtain the following thresholds:

$$V_{ThL} = \left(\frac{R1}{(R1 + R2)} \right) V_{OL} \quad (4)$$

$$V_{ThH} = \left(\frac{R1}{(R1 + R2)} \right) V_{OH}$$

Hardware Setup:

Build the following breadboard circuit for the inverting hysteresis comparator.

Procedure:

Use the first waveform generator as source V_{IN} to provide a 6 V amplitude peak-to-peak, 1 kHz sine wave excitation to the circuit. Supply the op amp to ± 5 V from the power supply. Configure the scope so that the input signal is displayed on Channel 1 and the output signal is displayed on Channel 2.

A plot example is presented in Figure 10.

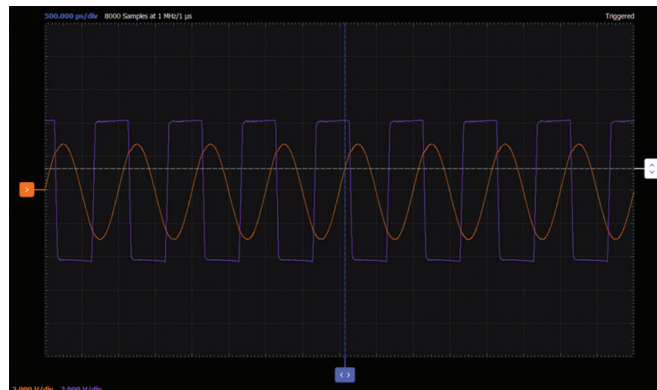


Figure 10. Inverting hysteresis comparator waveform.

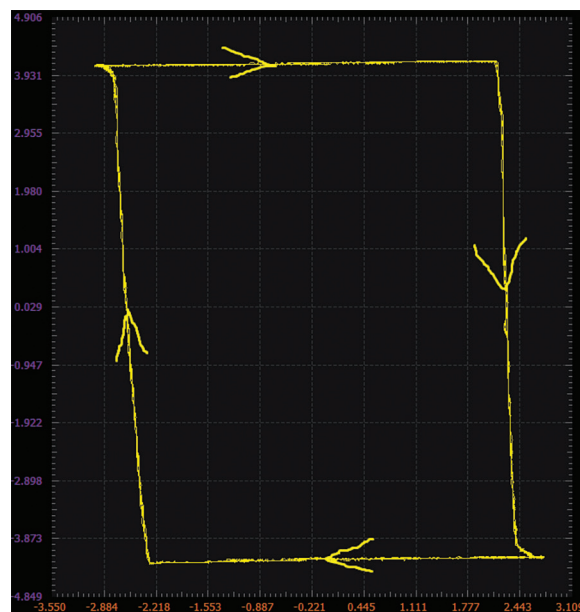


Figure 11. Inverting hysteresis comparator XY plot.

In Figure 11, you can observe the voltage transfer characteristic of the noninverting hysteresis comparator (the arrows drawn indicate the flow of the signal with respect to the thresholds). Compare the computed threshold voltage values with the measured ones.

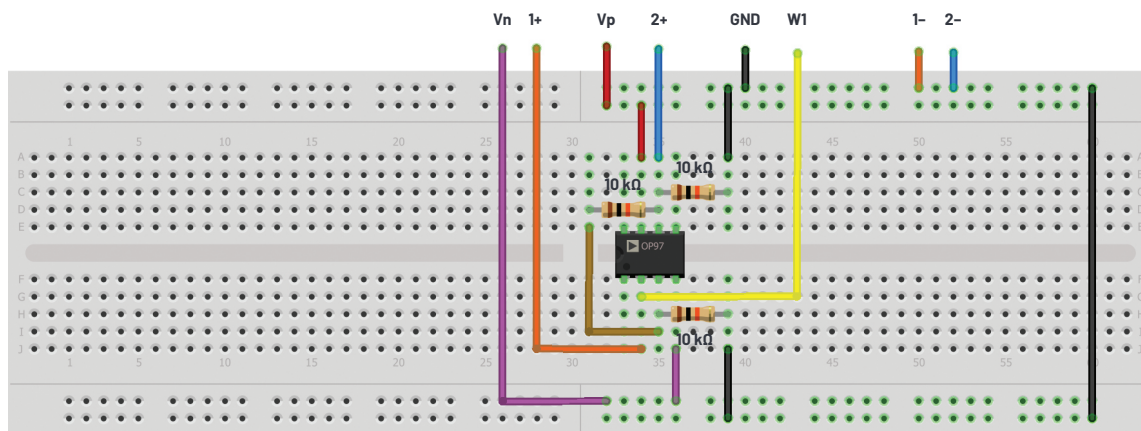


Figure 9. Inverting hysteresis comparator breadboard circuit.

Inverting Hysteresis Comparator with Asymmetric Thresholds

Background:

Consider the circuit presented in Figure 12.

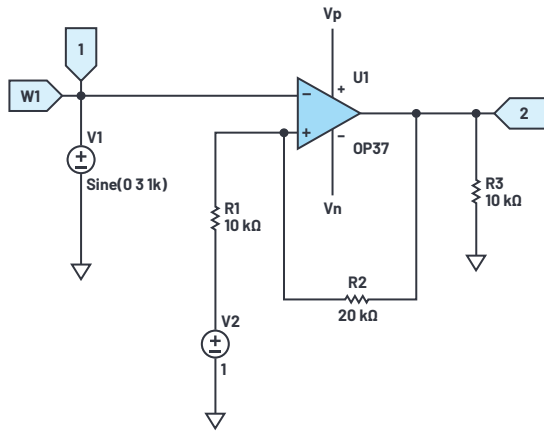


Figure 12. Inverting hysteresis comparator with asymmetric thresholds.

For the inverting comparator with asymmetric thresholds circuit in Figure 12, an additional reference voltage V_{REF} is used. Resistors R1 and R2 form a voltage divider network across the comparator providing the positive feedback with part of the output voltage appearing at the noninverting input, along with a part of the V_{REF} going through the same divider.

We can compute the threshold voltages as follows:

$$v_D = v^+ - v^- = \left(\frac{R1}{(R1 + R2)} \right) v_{OUT} + \left(\frac{R2}{(R1 + R2)} \right) V_{REF} - v_{IN} \quad (5)$$

Considering $V_D = 0$, $V_{IN} \rightarrow V_{Th}$, we obtain the following thresholds:

$$V_{ThL} = \left(\frac{R1}{(R1 + R2)} \right) V_{OL} + \left(\frac{R2}{(R1 + R2)} \right) V_{REF} \quad (6)$$

$$V_{ThH} = \left(\frac{R1}{(R1 + R2)} \right) V_{OH} + \left(\frac{R2}{(R1 + R2)} \right) V_{REF}$$

Hardware Setup:

Build the following breadboard circuit for the inverting hysteresis comparator.

Procedure:

Use the first waveform generator as source V_{IN} to provide a 6 V amplitude peak-to-peak, 1 kHz sine wave excitation to the circuit and second waveform generator as a constant 2 V voltage reference. Supply the op amp to ± 5 V from

the power supply. Configure the scope so that the input signal is displayed on Channel 1 and the output signal is displayed on Channel 2.

A plot example is presented in Figure 14.

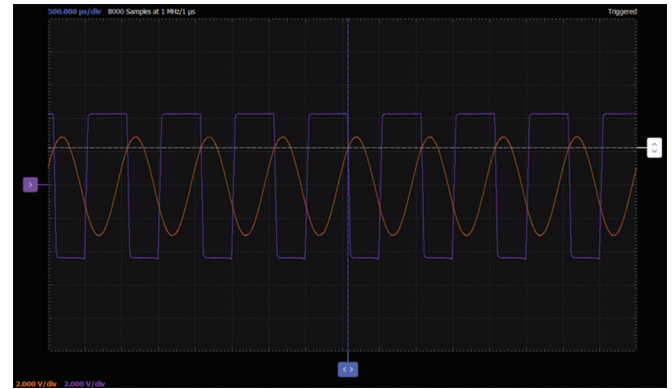


Figure 14. Inverting hysteresis comparator with asymmetric thresholds waveform.

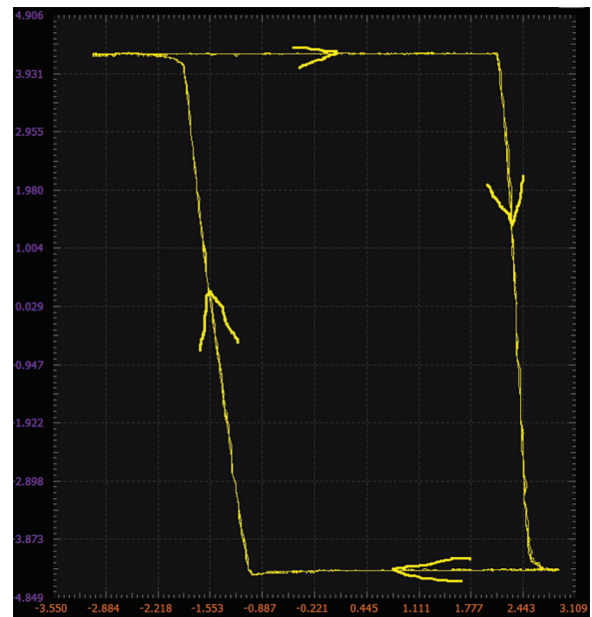


Figure 15. Inverting hysteresis comparator with asymmetric thresholds XY plot.

In Figure 15, you can observe the voltage transfer characteristic of the non-inverting hysteresis comparator (the arrows drawn indicate the flow of the signal with respect to the thresholds). Compare the computed threshold voltage values with the measured ones.

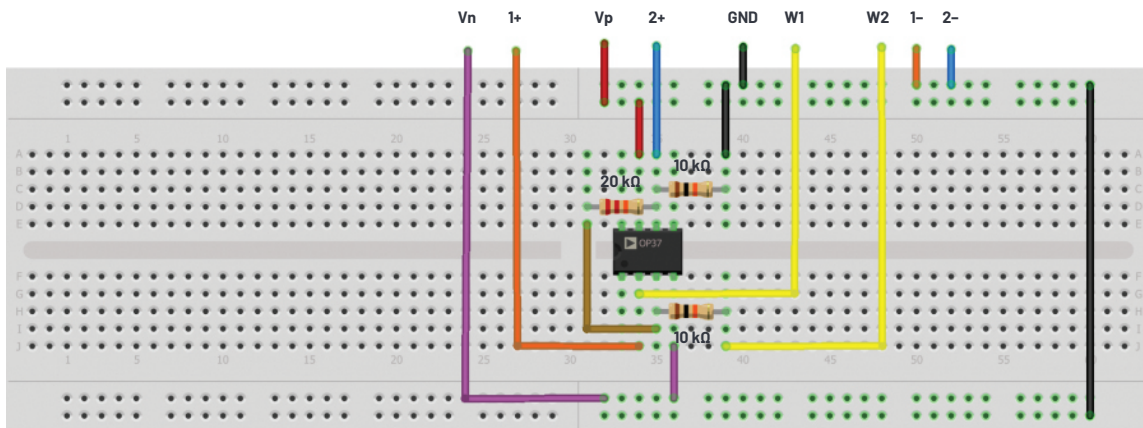


Figure 13. Inverting hysteresis comparator with asymmetric thresholds breadboard.

Question:

Compute the threshold voltages for all four comparator setups (simple, noninverting hysteresis, inverting hysteresis, and asymmetric thresholds) and compare the results with the ones obtained from the experimental setups.

Extra Activities

For experimenters who finish early or want an additional challenge, see if you can modify the comparator circuit using your red and green LEDs (from the last lab) at the output so that the red LED lights for negative voltages and the green LED lights for positive voltages. Turn down the frequency to 1 Hz (or less) so you can see them turn on-and-off in real time. Don't forget that the LEDs will need a current-limiting resistor so that the current through it is no more than 20 mA.

You can also extend the above example to a circuit with multiple voltage levels as the circuit presented in Figure 16.

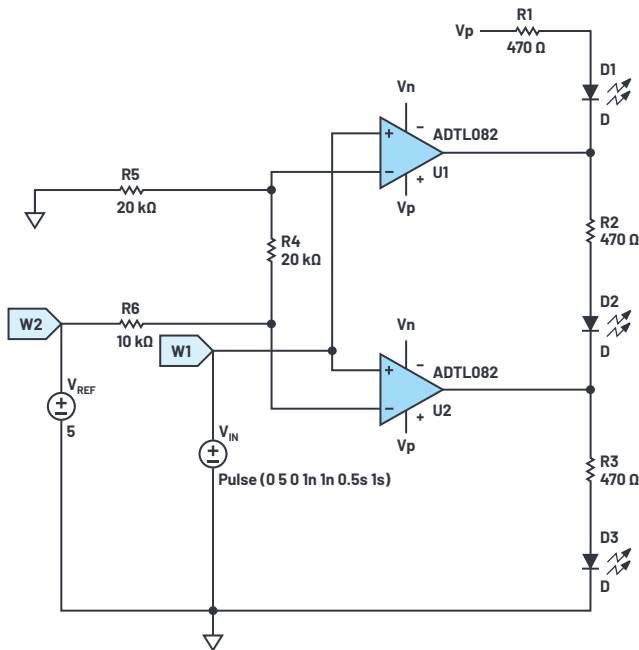


Figure 16. Voltage level indicator using LEDs.

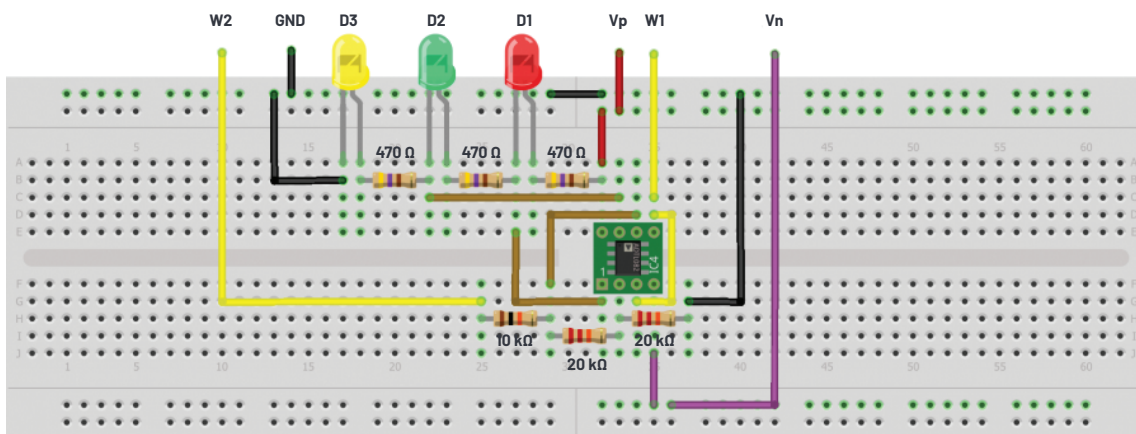


Figure 17. Voltage level indicator using LEDs.

Materials:

- ▶ ADALM2000 active learning module
- ▶ Solderless breadboard and jumper wire kit
- ▶ Three 470 Ω resistor
- ▶ One 10 k Ω resistor
- ▶ Two 20 k Ω resistor
- ▶ Three LEDs (red, green, yellow)
- ▶ One ADTL082 (two integrated op amps)

The circuit uses a divider (R_1 , R_2 , R_3) to obtain one threshold for each of the two comparators. Based on these thresholds and the input voltage, one LED (D_1 , D_2 , D_3) at a time will be on.

Exercises:

- ▶ Compute the threshold voltages according to the circuit in Figure 16. Determine which LED will be on for each input voltage range.
- ▶ Build the breadboard circuit. Supply the op amp to ± 5 V from the power supply. Use the first channel of the signal generator to generate the variable input voltage (V_{IN}) and the second channel to generate the 5 V constant reference voltage.

Vary the input voltage from 0 V to 5 V and observe the LEDs' behavior.

This type of circuit is also known as a window comparator. An application on this subject can be found in the activity: [Temperature Control Using Window Comparator](#).

You can find more details at the [StudentZone blog](#).



About the Author

Doug Mercer received his B.S.E.E. degree from Rensselaer Polytechnic Institute (RPI) in 1977. Since joining Analog Devices in 1977, he has contributed directly or indirectly to more than 30 data converter products and he holds 13 patents. He was appointed to the position of ADI Fellow in 1995. In 2009, he transitioned from full-time work and has continued consulting at ADI as a Fellow Emeritus contributing to the Active Learning Program. In 2016 he was named Engineer in Residence within the ECSE department at RPI. He can be reached at doug.mercer@analog.com.



About the Author

Antoni Miclaus is a system applications engineer at Analog Devices, where he works on ADI academic programs, as well as embedded software for Circuits from the Lab®, QA automation, and process management. He started working at Analog Devices in February 2017 in Cluj-Napoca, Romania. He is currently an M.Sc. student in the software engineering master's program at Babes-Bolyai University and he has a B.Eng. in electronics and telecommunications from Technical University of Cluj-Napoca. He can be reached at antoni.miclaus@analog.com.